

Dataflow SystemVerilog

- **Program** functions as high level expressions
 - Program logical and arithmetic expressions that describe what functions to implement
 - Wide selection of available operators (logical, arithmetic, shift, etc.)
- **Synthesize** a circuit from the expressions
 - Convert (synthesize) arithmetic expressions to logic equations
 - Convert (synthesize) logic equations to gates
 - Let the synthesizer minimize logic
- Significantly reduces time to design logic circuits
 - Focus on **what** the high level logic and arithmetic that you need, and **not how** it is implemented.
 - Design **productivity** is much higher than designing with gates
 - **Less risk** of errors and less debugging

Dataflow "assign" statement

- `assign <wire/port> = <dataflow expression>;`
- SystemVerilog module can contain a mix of structural SystemVerilog statements *and* dataflow "assign" statements
- "assign" statement operates concurrently with the other statements
 - Demand driven semantics: *the ordering of the assign statements does not matter*

Dataflow "assign" statement

- Wide variety of operators that can be used within an "assign" statement
 - Constant Assignment
 - Bitwise logic
 - Logic reduction
 - Arithmetic
 - Shift
 - Concatenate
 - Relational
 - Logical
 - Conditional operations

| Operator Type | Operator Symbol | Operation Performed | # of Operands | Comments |
|---------------|-----------------|---------------------|---------------|-------------------------------|
| Arithmetic | *, /, +, - | As expected | 2 | * and / take LOTS of hardware |
| | % | Modulo | 2 | |
| Logical | ! | Logic NOT | 1 | As in C |
| | && | Logic AND | 2 | As in C |
| | | Logic OR | 2 | As in C |
| Bitwise | ~ | Bitwise NOT | 1 | As in C |
| | & | Bitwise AND | 2 | As in C |
| | | Bitwise OR | 2 | As in C |
| | ^ | Bitwise XOR | 2 | As in C |
| | ~^ | Bitwise XNOR | 2 | |
| Relational | <, >, <=, >= | As expected | 2 | As in C |
| Equality | ==, != | As expected | 2 | As in C |
| Reduction | & | Red. AND | 1 | Multi-bit input |
| | ~& | Red. NAND | 1 | Multi-bit input |
| | | Red. OR | 1 | Multi-bit input |
| | ~ | Red. NOR | 1 | Multi-bit input |
| | ^ | Red. XOR | 1 | Multi-bit input |
| | ~^ | Red. XNOR | 1 | Multi-bit input |
| Shift | << | Left shift | 2 | Fill with 0's |
| | >> | Right shift | 2 | Fill with 0's |
| Concat | { } | Concatenate | Any number | |
| Replicate | {{ }} | Replicate | Any number | |
| Cond | ?: | As expected | 3 | As in C |

| Higher precedence |
|------------------------|
| Unary -, unary +, !, ~ |
| *, /, % |
| +, - |
| <<, >> |
| <, <=, >, >= |
| ==, != |
| &, ~& |
| ^, ~^ |
| , ~ |
| && |
| |
| ?: |
| Lower precedence |

Constant Assignment

- Assign a constant value to a wire
- Example:

```
logic [7:0] Q;
```

```
assign Q = 8'h3F;
```

SystemVerilog Bitwise Logical Operators


- Perform Boolean operation on single- or multi-bit signals

| Operator | Function | # Operands |
|----------|--------------|------------|
| ~ | Bitwise NOT | 1 |
| & | Bitwise AND | 2 |
| | Bitwise OR | 2 |
| ^ | Bitwise XOR | 2 |
| ~^ | Bitwise XNOR | 2 |


Multi-Bit Logical Operators

```
logic [3:0] A,B;  
assign A = 4'b0101;  
assign B = 4'b1101;
```


```
assign Q = A&B;
```

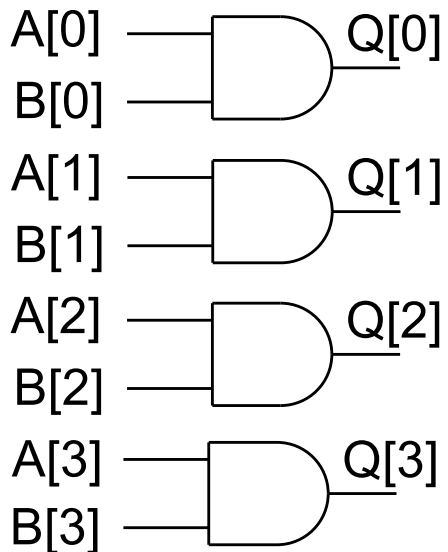


```
assign Q = A|B;
```

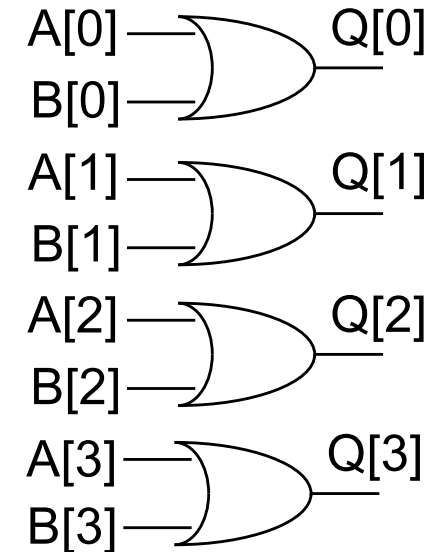

```
assign Q = A^B;
```

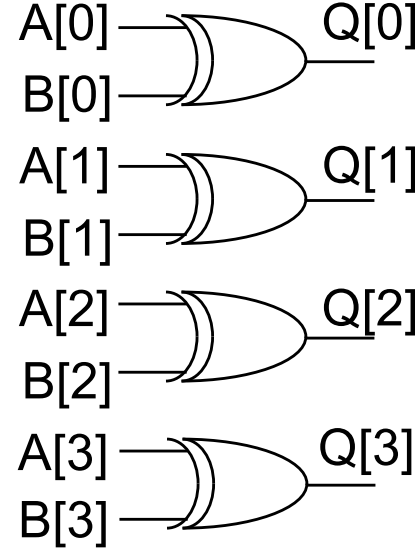


```
assign Q = ~A;
```

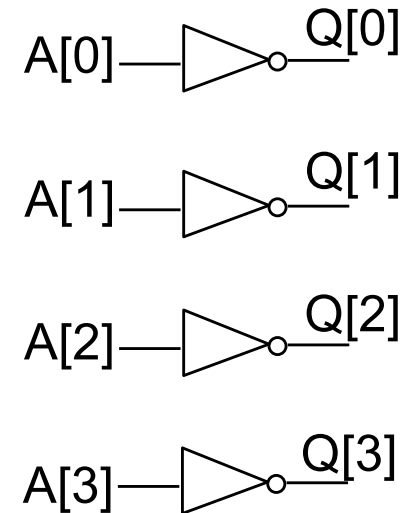

Reduction Operators

- Single (unary) operand operators that operate on multi-bit signals
 - Reduces a multi-bit wire to a single-bit result


| Operator | Function | # Operands |
|----------|-----------|------------|
| & | Red. AND | 1 |
| ~& | Red. NAND | 1 |
| | Red. OR | 1 |
| ~ | Red. NOR | 1 |
| ^ | Red. XOR | 1 |
| ~^ | Red. XNOR | 1 |

 


Reduction Operators

| Operator | Function | # Operands |
|----------|-----------|------------|
| & | Red. AND | 1 |
| ~& | Red. NAND | 1 |
| | Red. OR | 1 |
| ~ | Red. NOR | 1 |
| ^ | Red. XOR | 1 |
| ~^ | Red. XNOR | 1 |


Q is one bit

 


`assign Q = &A;`

 


`assign Q = |A;`

 


`assign Q = ^A;`

 


`assign Q = ~&A;`

 

`assign Q = ~|A;`

 

`assign Q = ~^A;`

 

Arithmetic Operators

- Performs 2's complement arithmetic
 - Generates a multi-bit result

| Operator | Function | # Operands | |
|----------|----------------|------------|-----------|
| - | Negate | 1 | |
| + | Addition | 2 | |
| - | Subtraction | 2 | |
| * | Multiplication | 2 | |
| / | Division | 2 | |
| % | Modulo | 2 | remainder |

```
logic [7:0] A,B,O;  
assign O = A+B;  
assign O = A%3;
```

Generates all logic necessary to implement 2's complement arithmetic. **Avoid using '*' and '/' (may not synthesize)**

← Remainder of A divided by 3



Shift Operators

- Shift signals

| Operator | Function | # Operands |
|----------|-------------|------------|
| << | Left Shift | 2 |
| >> | Right Shift | 2 |

- Fills vacated bits with zeros
  
```
logic [7:0] A,F,G;
assign A = 8'b01010011;
```



```
assign F = A<<2; → assign F = {A[5:0], 2'b00};
assign G = A>>2; → assign G = {2'b00, A[7:2]};
```

Shift Operators

Shift to the left : multiply by 2 per digit shifted

$$0010\ 0001 = 33$$

$$0100\ 0010 = 66 = 33 \times 2$$

$$1000\ 0100 = 132 == 66 \times 2$$

Shift to the right : divide by 2 per digit shifted

$$0010\ 0001 = 33$$

$$0001\ 0000 = 16 = 33/2$$

$$0000\ 1000 = 8 == 33/4$$

Concatenate Operators

| Operator | Function |
|----------|-----------------------|
| {x, y} | Concatenate x and y |
| N {x} | Replicate 'x' N times |

Concatenation and Replication Operators

`{x, y}` *Concatenate x to y*
`N{x}` *Replicate x N-times*

```
logic[3:0] x, y;  
logic[7:0] z, q, w, t;  
logic[31:0] m, n;
```

```
assign x = 4'b1100;  
assign y = 4'b0101;  
assign z = {x, x};     // z is 8'b11001100  
assign q = {x, y};     // q is 8'b11000101  
assign w = {4'b1101, y};     // w is 8'b11010101  
assign t = {2{x}};     // same as {x, x}  
assign m = {{4{x}}, {2{q}}};  
         // m is 32'b11001100110011001100010111000101
```

Relational Operators

- Comparing two operands against each other
 - Returns a logical '1' or '0' (representing T and F)

| Operator | Function | # Operands |
|----------|-----------------------|------------|
| == | Equal | 2 |
| != | Not Equal | 2 |
| < | Less Than | 2 |
| <= | Less Than or equal | 2 |
| > | Greater Than | 2 |
| >= | Greater Than or equal | 2 |

```
always_comb
```

```
  If (w <= 4'b1001)
```

```
    A = 0;
```

```
  else
```

```
    A = 1;
```

```
always_comb
```

```
  If (w == 4'd9)
```

```
    A = 0;
```

```
  else
```

```
    A = 1;
```

```
always_comb
```

```
  If (w == 9)
```

```
    A = 0;
```

```
  else
```

```
    A = 1;
```

```
always_comb
```

```
  If (X&Y != Z)
```

```
    A = 0;
```

```
  else
```

```
    A = 1;
```

Logical Operators

- Operate on logical (rather than bit) values
 - Returns a logical '1' or '0' (representing T and F)

| <u>Operator</u> | <u>Function</u> | <u># Operands</u> |
|-----------------|-----------------|-------------------|
| ! | Not | 1 |
| && | And | 2 |
| | Or | 2 |

```
always_comb
```

```
  If (w <= 4'b1001 && X&Y != Z)
```

```
    A = 0;
```

```
else
```

```
  A = 1;
```

```
assign A = (w == 4'b1001 || X&Y != Z) ? 0 : 1;
```


Conditional Operator

- Performs like a 2-to-1 multiplexor
 - "If-then-else" operator

| Operator | Function | # Operands |
|----------|-------------|------------|
| ? : | Conditional | 3 |

`<logical expression> ? <result if true> : <result if false>`

```
assign o = A>B ? C : 4'hF;
```

↙
O = C if A > B
O = 4'hF if A <= B

Operator Precedence

- Similar to C

| Higher precedence |
|------------------------|
| Unary -, unary +, !, ~ |
| *, /, % |
| +, - |
| <<, >> |
| <, <=, >, >= |
| ==, != |
| &, ~& |
| ^, ~^ |
| , ~ |
| && |
| |
| ?: |
| Lower precedence |

A Dataflow MUX - Version 1

```
module mux21(  
    input wire logic sel, a, b,  
    output logic q);  
  
    assign q = (~sel & a) | (sel & b);  
endmodule
```

*Much simpler, less typing, familiar C-like syntax.
Synthesizer turns it into optimized gate-level design.*

A Dataflow MUX - Version 2

```
module mux21(  
    input wire logic sel, a, b,  
    output logic q);  
  
    assign q = sel ? b : a;  
endmodule
```

Even simpler, uses C-like ternary (?:) construct

Bitwise vs. Logic Operators

- Similar to C

```
assign q = ((a<4'b1101) && ((c&4'b0011) !=0)) ? 1'b0:1'b1;
```


Pseudo-code (not real SystemVerilog):

if (a<4'b1101 && (c&4'b0011) != 0) then

q <= '0';

else

q <= '1';

 

Use &&, ||, ! for 1-bit quantities (results of comparisons)

Use &, |, ~ for bit-by-bit logical operations

A Note on Matching Widths

- This is a valid 2:1 MUX statement:

```
logic a, b, sel, q;  
assign q = (~sel & a) | (sel & b);
```

- But the following is not:

```
logic[3:0] a, b, q;  
logic sel;  
assign q = (~sel & a) | (sel & b);
```

Why?

More On Matching Wire Widths

- This is an acceptable substitute:

```
logic[3:0] a, b, q;  
logic sel;  
assign q = ({4{~sel}}&a) | ({4{sel}}&b);
```

- It turns the `sel` and `~sel` values into 4-bit versions for AND-ing and OR-ing

- A better version:

```
logic[3:0] a, b, q;  
logic sel;  
assign q = sel ? b : a;
```

Design Example: A 2:4 Decoder

```
module decode24 (  
    output logic[3:0] q,  
    input wire logic[1:0] a);  
  
    assign q = (4'b0001) << a;  
endmodule
```

Can you see how to make a 3:8 or 4:16 decoder in the same fashion?

a is a two-bit number from 0~3. If a = 0, what is q ?
 If a = 1, what is q ?
 If a = 2, what is q ?
 If a = 3, what is q ?

Four Functions

```
module FourFunctions(  
    input wire logic A,B,C,  
    output logic O1,O2,O3,O4);  
  
    assign O1 = (A&C) | (~A&B);           // AC+A'B  
    assign O2 = (A|~C) &B&C;             // (A+C')BC  
    assign O3 = (A&~B) +C;               // AB'+C  
    assign O4 = ~(A&B) +~(~C&~B);       // (AB)' + (B'C')'  
  
endmodule
```

Lab 4 - Arithmetic

```


module arithmetic(
  input wire logic[15:0] sw,
  input wire logic btnl, btnr,
  output logic[8:0] led);

  logic[8:0] a,b;

  assign b = {sw[7],sw[7:0]};
  assign a = (btnl == 1'b1) ? 9'd0 : {sw[15],sw[15:8]};
  assign led = (btnr == 1'b1) ? a-b : a+b;

endmodule


```

 

| | | | |
|------|--------|----|--|
| sw | Input | 16 | Switches (sw[15:8] = A input, sw[7:0] = B) |
| btnl | Input | 1 | Left Button (Zero A operand) |
| btnr | Input | 1 | Right Button (negation of B operand) |
| led | Output | 9 | LED signals (result) |

Lab 5 - Seven Segment Decoder


```
module seven_segment(  
    input wire logic[3:0] data,  
    output logic[6:0] segment);  
    assign segment =  
        (data == 0) ? 7'b1000000 :  
        (data == 1) ? 7'b1111001 :  
        (data == 2) ? 7'b0100100 :  
        (data == 3) ? 7'b0110000 :  
        (data == 4) ? 7'b0011001 :  
        (data == 5) ? 7'b0010010 :  
        (data == 6) ? 7'b0000010 :  
        (data == 7) ? 7'b1111000 :  
        (data == 8) ? 7'b0000000 :  
        (data == 9) ? 7'b0010000 :  
        (data == 10) ? 7'b0001000 :  
        (data == 11) ? 7'b0000011 :  
        (data == 12) ? 7'b1000110 :  
        (data == 13) ? 7'b0100001 :  
        (data == 14) ? 7'b0000110 :  
        7'b0001110;  
endmodule
```

 

Multi-bit Design and Parameterization

A Dataflow MUX - Multi-Bit
 
```
module mux21 (  
    input logic sel,  
    input logic[15:0] a, b,  
    output logic[15:0] q);  
  
    assign q = sel ? b : a;  
endmodule
```



Key Ideas:

The predicate must evaluate to true or false (1 or 0)

The parts getting assigned must be all same widths.

A Dataflow MUX - Parameterized Width

```
module mux21n #(parameter WID = 16) (  
    input wire logic sel,  
    input wire logic[WID-1:0] a, b,  
    output logic[WID-1:0] q);  
  
    assign q = sel ? b : a;  
endmodule
```

- By default, this is now a 16-bit wide MUX.
- When instantiating, the default value of 16 can be overridden:

```
mux21n M1(q, sel, a, b);           // Instance a 16-bit version  
mux21n M0 #(4) (q, sel, a, b);    // Instance a 4-bit version
```

Does this work for a 1-bit MUX?

4:1 MUX - Method 1

```
module mux41n #(parameter WID=16) (  
    input wire logic[1:0] sel,  
    input wire logic[WID-1:0] a, b, c, d,  
    output logic[WID-1:0] q  
);  
  
    logic[WID-1:0] tmp1, tmp2;  
  
    mux21n M0 #(WID) (tmp1, sel[0], a, b);  
    mux21n M1 #(WID) (tmp2, sel[0], c, d);  
    mux21n M2 #(WID) (q, sel[1], tmp1, tmp2);  
endmodule
```

If the mux21n cells are parameterizable for bit-width this works...
If not, it doesn't work...

4:1 MUX - Method 2

```
module mux41 #(WID=16) (  
    input logic[1:0] sel,  
    input logic[WID-1:0] a, b, c, d,  
    output logic[WID-1:0] q  
);  
  
    assign q = (sel == 2'b00) ? a:  
               (sel == 1)      ? b:  
               (sel == 2'b10) ? c:  
               d;  
  
endmodule
```

Cascaded ?: operators form an if-then-else structure

Note how `sel` can be compared to bit patterns (`2'b00`) or to decimal numbers (`1`)